BBE

PROVISIONAL ANSWER KEY

Name of The Post Assistant Engineer (Electrical), Class-2

 Advertisement No
 21/2021-22

 Preliminary Test Held On
 03-10-2021

 Que. No.
 001-300

 Publish Date
 04-10-2021

 Last Date to Send Suggestion (S)
 12-10-2021

Instructions / মুথলা (Physical Submission)

Candidate must ensure compliance to the instructions mentioned below, else objections shall not be considered: -

- (1) All the suggestion should be submitted in prescribed format of suggestion sheet PHYSICALLY.
- (2) Question wise suggestion to be submitted in the prescribed format (Suggestion Sheet) published on the website.
- (3) All suggestions are to be submitted with reference to the Master Question Paper with provisional answer key (Master Question Paper), published herewith on the website. Objections should be sent referring to the Question, Question No. & options of the Master Question Paper.
- (4) Suggestions regarding question nos. and options other than provisional answer key (Master Question Paper) shall not be considered.
- (5) Objections and answers suggested by the candidate should be in compliance with the responses given by him in his answer sheet. Objections shall not be considered, in case, if responses given in the answer sheet /response sheet and submitted suggestions are differed.
- (6) Objection for each question shall be made on separate sheet. Objection for more than one question in single sheet shall not be considered & treated as Cancelled.
- (7) Candidate who is present in the exam entitled to submit the objection/(s).
- (8) Candidate should attach copy of his/her OMR (Answer sheet) with objection/(s).

ઉમેદવારે નીયેની સૂયનાઓનું પાલન કરવાની તકેદારી રાખવી, અન્યથા વાંધા-સૂયન અંગે કરેલ રજૂઆતો ધ્યાને લેવાશે નહીં

- (1) ઉમેદવારે વાંધા-સૂચનો નિયત કરવામાં આવેલ વાંધા-સૂચન પત્રકથી રજૂ કરવાના રહેશે.
- (2) ઉમેદવારે પ્રશ્નપ્રમાણે વાંધા-સૂયનો રજૂ કરવા વેબસાઈટ પર પ્રસિધ્ધ થયેલ નિયત વાંધા-સૂયન પત્રકના નમુનાનો જ ઉપયોગ કરવો.
- (3) ઉમેદવારે પોતાને પરીક્ષામાં મળેલ પ્રશ્નપુસ્તિકામાં છપાયેલ પ્રશ્નક્રમાંક મુજબ વાંધા-સૂચનો રજૂ ન કરતા તમામ વાંધા-સૂચનો વેબસાઈટ પર પ્રસિધ્ધ થયેલ પ્રોવિઝનલ આન્સર કી (માસ્ટર પ્રશ્નપત્ર)ના પ્રશ્ન ક્રમાંક મુજબ અને તે સંદર્ભમાં રજૂ કરવા.
- (4) માસ્ટર પ્રશ્નપત્ર માં નિર્દિષ્ટ પ્રશ્ન અને વિકલ્પ સિવાયના વાંધા-સૂચન ધ્યાને લેવામાં આવશે નહી.
- (5) ઉમેદવારે જે પ્રશ્નના વિકલ્પ પર વાંધો રજૂ કરેલ છે અને વિકલ્પ રૂપે જે જવાબ સૂયવેલ છે એ જવાબ ઉમેદવારે પોતાની ઉત્તરવહીમાં આપેલ હોવો જોઈએ. ઉમેદવારે સૂયવેલ જવાબ અને ઉત્તરવહીનો જવાબ ભિન્ન હશે તો ઉમેદવારે રજૂ કરેલ વાંધા-સૂયન ધ્યાનમાં લેવાશે નહી.
- (6) એક પ્રશ્ન માટે એક જ વાંધા-સૂચન પત્રક વાપરવું. એક જ વાંધા-સૂચન પત્રકમાં એકથી વધારે પ્રશ્નોની રજૂઆત કરેલ હશે તો તે અંગેના વાંધા-સૂચનો ધ્યાને લેવાશે નહી.
- (7) પરીક્ષામાં હાજર રહેલ ઉમેદવાર જ વાંધા સુચન રજુ કરી શકશે .
- (8) ઉમેદવારે વાંધા-સુચન સાથે પોતાની જવાબવહીની નકલ બિડાણ કરવાની રહેશે.

001.	પૃથ્વાના જમાન પકા કટલા જમાન પર ભારત દેશ આવેલ છ) :
	(A) 2.4%	(B) 3.4%
	(C) 4.4%	(D) 5.4%
002.	સેટેલાઈટ ડેટાની વીગતો મુજબ, ભારતમાં જંગલનો વિસ્તા	5
	(A) વધી રહેલ છે.	
	(B) ઘટી રહેલ છે.	
	(C) કોઈ વધ ઘટ નથી.	
	(D) ખુલ્લા જંગલો વધી રહ્યા છે પરંતુ આરક્ષીત જંગલ વિસ્ત	તાર ઘટી રહેલ છે.
003.	ધી રેડક્લીફ લાઈન (The Radcliffe line) એ ક્યા દેશો વ	વચ્ચેની સીમા રેખા છે ?
	(A) ભારત અને ચીન	(B) ભારત અને મ્યાનમાર
	ભારત અને પાકીસ્તાન	(D) ભારત અને અફઘાનીસ્તાન
004.	2011 ના સેન્સસ મુજબ સૌથી વધુ વસ્તી ધરાવતા ત્રણ રાજ	યો ક્યાં છે ?
	(A) ઉત્તર પ્રદેશ, મધ્ય પ્રદેશ, ગુજરાત	(B) ઉત્તર પ્રદેશ, મહારાષ્ટ્ર, બિહાર
	(C) મધ્યપ્રદેશ, મહારાષ્ટ્ર, ગુજરાત	(D) મધ્યપ્રદેશ, મહારાષ્ટ્ર, ઉત્તરપ્રદેશ
005.	ભારતની સને '2019-20' નાં વર્ષની	
	1. પર કેપીટા નેટ નેશનલ ઇન્કમ - (per capita net nati	onal income) રૂા 1,35,050 છે
	2. ભારતમાં સૌથી વધારે NSDP per capita ગોવા રાજ્ય	ની છે.
	ઉપરોક્ત વાક્યો ચકાસો.	
	(A) 1 વાક્ય યોગ્ય છે	(B) 2 વાક્ય યોગ્ય છે
	🔘 1 અને 2 વાક્યો યોગ્ય છે	(D) 1 અને 2 વાક્યો યોગ્ય નથી
006.	દેશની સેંચુરી (Sanctuary) અને આરક્ષીત જંગલો અને રા	જ્યની જોડી ઓ પૈકી કઈ જોડી યોગ્ય નથી ?
	(A) જીમ કોર્બેટ નેશનલ પાર્ક - ઉત્તરાખંડ	
	(B) નાનમંગલમ (Nanmangalam) રીઝર્વ ફોરેસ્ટ - તાર્મ	<u>ો</u> લનાડુ
	🔘 અમરામ બાલમ (Amaram balam) રીઝર્વ ફોરેસ્ટ	- કર્નાટક
	(D) કુકરેલ (Kukrail) રીઝર્વ ફોરેસ્ટ - ઉત્તર પ્રદેશ.	
007.	આદિજાતિના મેળાઓ-ઉત્સવો અને જીલ્લાની જોડી પૈકી કઈ	ેજોડીઓ યો ^{ગ્} ય છે.
	1. ભાગું રિયા - વડોદરા	
	2. ગોળ ગધેડાનો મેળો - દાહોદ	
	3. ચિત્ર - વિચિત્ર મેળો - બનાસકાંઠા	
	4. નાગ ધરાનો મેળો - જુનાગઢ	_
	(A) 1 અને 3	(B) 1 અને 2
	(C) 1 અને 4	(D) 2 અને 3

- 008. 1. ગુજરાત રાજ્યમાં 14 આદિવાસી જીલ્લાઓ આવેલ છે.
 - 2. ગુજરાતમાં 15 અનુસૂચિત જનજાતિઓ અને 7 આદિમ જુથો છે.

ઉપરના વાક્યો ચકાસો.

- (A) માત્ર 1 વાક્ય યોગ્ય છે
- (B) માત્ર 2 વાક્ય યોગ્ય છે
- (C) 1 અને 2 બંન્ને વાક્યો યોગ્ય છે
- (D) 1 અને 2 બંન્ને વાક્યો યોગ્ય નથી
- 009. ભારતના નૃત્યો અને તેના પ્રદેશોને જોડો.
 - 1. સનથાલી નૃત્ય
 - 2. બીહુ નૃત્ય
 - 3. ઘુમર નૃત્ય
 - 4. આહીરી નૃત્ય
 - (A) 1 d, 2 a, 3 b, 4 c
 - (C) 1 b, 2 c, 3 d, 4 a

- a. મધ્યપ્રદેશ
- h. પશ્ચિમ બંગાળ
- c. આસામ
- d. રાજસ્થાન
- (B) 1 c, 2 d, 3 a, 4 b
- (D) 1 a, 2 b, 3 c, 4 d
- 010. 1. ઈન્નોર (Ennore) બંદર તામીલનાડુ ખાતે આવેલ છે. તે કોર્પોરેટ ક્ષેત્રનું પ્રથમ બંદર છે ત્યાંથી ચા, કોફી અને મસાલાની નીકાસ થાય છે.
 - 2. મેંગલોર બંદર કર્નાટકમાં આવેલ છે અને બારેમાસ, ઉંડું પાણી હોય તેવું બંદર છે તે કર્નાટકનું એક માત્ર મેજર પોર્ટ છે જ્યાંથી આર્યન ઓર (Iron ore)ની નીકાસ થાય છે
 - (A) 1 વાક્ય યોગ્ય છે
 - (B) 2 વાક્ય યોગ્ય છે
 - (C) 1 અને 2 બંન્ને વાક્યો યોગ્ય છે
 - (D) 1 અને 2 બંન્ને વાક્યો યોગ્ય નથી.
- 011. થીલ્લના (Thillana) એ ક્યા નૃત્યનો એક ભાગ છે ?
 - (A) કુચીપુડી (Kuchipudi)
 - (B) ઓડીસી (Odissi)
 - (C) ભરતનાટ્યમ (Bharatanatyam)
 - (D) કથ્થક (Kathak)
- 012. ભારતના રાજ્યો અને તેની રાજધાનીને યોગ્ય રીતે જોડો.
 - 1. અરૂણાચલ પ્રદેશ
 - 2. છત્તીસગઢ
 - 3. ઝારખંડ
 - 4. નાગાલેન્ડ
 - (A)1 a, 2 b, 3 c, 4 d
 - (C) 1 c, 2 d, 3 a, 4 b

- a. ઇટાનગર
- b. રાયપુર
- c. રાંચી
- d. કોહીમાં
- (B) 1 b, 2 c, 3 d, 4 a
- (D) 1 d, 2 a, 3 b, 4 c

IVI		
013.	કેન્દ્ર શાસિત પ્રદેશો અને તેની રાજધાનીઓની જોડીઓ પૈકી (A) અંદામાન નિકોબાર - પોર્ટ બ્લેયર (B) દાદરા તથા નગર હવેલી અને દમણ અને દીવ - દમણ (C) લક્ષદ્વીપ -કરાવતી (D)પુડુચેરી - ચેન્નઈ	કઈ જોડી યોગ્ય નથી ?
014.	નેશનલ મ્યુઝીયમ - દીલ્હી દ્વારા લાઈફ ઈન મીનીએચર (Li (A) માયક્રોસોફ્ટ (C) ફેસબુક	fe in Miniature) પ્રોજેકટ કઈ કંપની સાથે શરૂ કરેલ છે ? (B) ગુગલ (D) એમેઝોન
015.	ચાર-ચાપોરી (Char - Chapori) કે જે હાલમાં સમાચારમ (A) નાગાલેન્ડ (C) છત્તીસગઢ	i હતા તે ક્યા રાજ્યમાં આવેલ છે ? (B) અરૂણાચલ પ્રદેશ D)આસામ
016.	"સારે જહાસે અચ્છા" ગીતના રચનાકાર કોણ છે ? (A) જયદેવ (C) બંકીમચંદ્ર ચટ્ટોપાધ્યાય	(B) મહમદ ઈકબાલ (D) રવીન્દ્રનાથ ટાગોર
017.	ભારતમાં અગ્રેજી લેખકો અને તેઓની કૃતિની જોડી પૈકી કઈ (A) અનીતા દેસાઈ - The Village by The Sea, The P B) મુલ્ક રાજઆનંદ - The Dark Room (1938), Mr. (C) વિક્રમ શેઠ - An Equal Music, A Suitable Girl (D) ખુશવંત સીંગ - A Train to Pakistan in 1956, Th	eacock Garden Sampath (1945)
018.	હીન્દી ભાષામાં લેખકો અને તેઓની કૃતિ ને યોગ્ય રીતે જોડો 1. હરીવંશરાય બચ્ચન 2. રામધારી સીંધ દીનકર 3. અમર ગોસ્વામી 4. સુર્યકાંત ત્રિપાઠી (A) 1 - c, 2 - d, 3 - a, 4 - b (C) 1 - d, 2 - a, 3 - b, 4 - c	. a. ગીતીકા, પ્રભાવતી b. મધુશાલા c. ઉવર્શી, નીલ કુસુમ d. ગુહારા, દુલ્હન B) 1 - b, 2 - c, 3 - d, 4 - a (D) 1 - b, 2 - d, 3 - c, 4 - a
019.	મધ્યપ્રદેશમાં આવેલ બાઘ (Bagh) ગામ ક્યા કારણસર પ્રખ (A) શિલ્પો (Sculptures) (B) સ્થાપત્ય (Architecture)	યાત છે ?

🔘 ગુફા પેઈન્ટિંગ (Cave painting)

(D) ધોધ (Waterfall)

	(C) દેવપાલ (Devapala)	(D) દેવપાલ - બીજો (Devapala 2)
	(A) ગોપાલા (Gopala)	B) ધર્મપાલ (Dharmapala)
026.	પાલા રાજાના (Pala Kings) વંશજો પૈકી વિક્રમશીલા	યુનિવર્સિટીની સ્થાપના કોણે કરેલ હતી ?
	C) રીગવેદ (Rigveda)	(D) અર્થવવેદ (Atharvaveda)
	(A) સામવેદ (Samveda)	(B) યજુર્વેદ (Yajurveda)
025.	નીચેના પૈકી ક્યો વેદ સૌથી જુનો વેદ છે ?	
	(C) રથા (Ratha)	(D) યાજના (Yajna)
	(A) શખા (Shakha)	B) ચમા (Chama)
024.	સ્કુલ-શાળા અથવા વેદોની અલગ અલગ શાખાઓ જે નામથી જાણીતા હતા ?	જગ્યાએ ભણાવવામાં આવતી હતી તે સ્થળ પ્રાચીન ભારતમાં કયા
	(A) ઉત્તરપ્રદેશ (C) રાજસ્થાન	(B) ગુજરાત (D) મધ્યપ્રદેશ
	દ્વારા શરૂ કરવામાં આવેલ છે ?	(B) 216/21 J
023.	•	ર્યના લોકોને ગુણવત્તા સભર ભોજન આપવામાં આવે છે તે ક્યા રાજ્ય
	(C) 2, 3 અને 4	(D) 1, 3 अने 4
	(A) 1, 2 અને 4	(B) 1, 2 અને 3
	4. ચિનુભાઈ ચંદુલાલ મોદી - શેષ	
	3. ઉમાશંકર જેઠાલાલ જોષી - વાસુકી	
	2. બળવંતરાય કલ્યાણરાય ઠાકોર - સેહની	
	1. મણિશંકર રત્નજી ભટ્ટ - કાંન્ત	
022.	લેખકો અને તેઓના ઉપનામની જોડીઓ પૈકી કઈ જોડી	ઓ યોગ્ય છે.
	()અનુષ્ટુપ	(D) મંદાક્રાન્તા
	(A) વંસતતિલકા	(B) શાર્દુલવિક્રીડિત
	આ કાવ્ય પંક્તિનો છંદ કયો છે ?	
	કૃષિક એ ઊઠી ત્યારે આવો બાપું કહી ઉભો''	
021.	''ત્યાંતો આવી પહોચ્યો એ અશ્વ સાથે યુવાન ત્યાં	
	D) નારાયણ સરોવર - અમરેલી	
	(C) ગોમતી તળાવ - વડોદરા	
	(B) હમીરસર તળાવ - કચ્છ	
020.	(A) નળ સરોવર - અમદાવાદ જીલ્લો	
020.	ગુજરાતના સરોવરો - અને સ્થળ/જીલ્લાની જોડીઓ પૈક	રી કઈ જોડી યોગ્ય નથી ?

036. 1946 નો ઇન્ડીયન નેશનલ આર્મી (INA) નો મુકદમામાં બચાવ પક્ષે નીચેના પૈકી ક્યા મહાનુભાવ વકીલ તરીકે ન હતા ?

(C) શ્રી સત્યેન્દ્રનાથ બોઝ

(A) શ્રી બલ્લુભાઇ દેસાઈ

(C) મહાત્મા ગાંધી

(D) શ્રી હરીગોવિંદ ખુરાના

(D) કૈલાશનાથ કાત્જુ

(B) શ્રી પંડીત જવાહરલાલ નહેરૂ

- 037. 1. સને 1951-1956 દરમ્યાન પ્રથમ પંચવર્ષીય યોજના શરૂ કરવામાં આવેલ, ખેતી વિકાસ તે યોજનાનો મુખ્ય હેતુ હતો.
 - 2. સને 1956-61 દરમ્યાન બીજી પંચવર્ષીય યોજના પી.સી. મહાલનોબીસ મોડેલ ઉપર આધારીત હતી, ઔદ્યોગીકરણ યોજનાનો મુખ્ય હેતુ હતો.

ઉપરોક્ત વાક્યો ચકાસો.

(A) 1 વાક્ય યોગ્ય છે

(B) 2 વાક્ય યોગ્ય છે

(C) 1 અને 2 વાક્યો યોગ્ય છે

- (D) 1 અને 2 વાક્યો યોગ્ય નથી
- 038. આતંરાષ્ટ્રીય વેપારમાં "BPD" એકમ કઈ વસ્તુ સાથે સબંધ ધરાવે છે ?
 - (A) લાઈવ સ્ટૉક અને મટન (Meat and Livestock)
 - (B) કિંમતી ધાતુઓ (Precious Metals)
 - (C) ઔદ્યોગીક વસ્તુઓ (Industrial Products)
 - D) ક્રુડ ઓઈલ (Crude Oil)
- 039. દેશમાં નાણાની પ્રવાહીતા (Liquidity in the system) ઘટાડવા માટે શાનો ઉપયોગ કરવામાં આવે છે ?
 - (A) રેપો રેટ (Repo rate)
 - (B) કેશ રીઝર્વ રેશીયો (Cash Reserve Ratio)
 - (C) પ્રાઈમ લેન્ડીગ રેટ (Prime Lending Rate)
 - (D) BPLR (Benchmark Prime Lending Rate)
- 040. હવાલા વ્યવહારો (Hawala Transactions) ક્યા કાયદાને કારણે પ્રતિબંધીત છે ?
 - (A) FERA

(B) FEMA

(C) FRBMA

- (D) AFSPA
- 041. ભારતમાંથી મધ (Honey) ની સૌથી વધારે આયાત કરનાર ક્યો દેશ છે ?
 - (A) અમેરીકા

(B) જર્મની

(C) ચીન

- (D) ઈટલી
- 042. દેશમાં અસમાનતા દુર કરવા રીડીસ્ટ્રીબ્યુશન પોલીસી (Redistribution Policy) અમલમાં મુકવામાં આવે છે. આ પોલીસીમાં કઈ બાબતનો સમાવેશ થાય છે ?
 - (A) પ્રોગ્રેસીવ ટેક્સ પોલીસી
 - (B) જમીન સુધારણા
 - (C) ગ્રામ વિકાસની યોજનાઓ
 - (D) ઉપરોક્ત બધીજ યોજના
- 043. સામાન્ય સંજોગોમાં ટુંકી મુદતનું ધિરાણ કેટલા સમય સુધીનું હોય છે ?
 - (A) 3 માસ

(B) 6 માસ

(C) 12 માસ

(D) 24 માસ

- 044. બેન્કોની રોકડની તરલતા (Cash in Hand) અને કુલ મિલકતો, ચોક્કસ રેશીયો માં રાખવામાં આવે છે આ રેશીયોને શું કહેવાય છે ?
 - (A) SBR (Statutory Bank Ratio)
 - (B) SLR (Statutory Liquid Ratio)
 - (C) CBR (Central Bank Ratio)
 - (D) CLR (Current Liquid Ratio)
- 045. ચલણના અવમૂલ્યનને કારણે, આખરે બજારમાં વસ્તુઓનો મુલ્યોમાં
 - (A) ધટાડો થશે
 - (B) વધારો થશે
 - (C) ખુબજ મોટા પ્રમાણમાં વધારો / ધટાડો થશે
 - (D) કોઈ અસર નહી થાય
- 046. 1. "આમુખ એ બંધારણનો ભાગ છે" એ બાબત કેશવાનંદ ભારતી કેસમાં, 13 માન. ન્યાયધીશો ની બેંચ દ્વારા આ બાબત નક્કી થયેલ હતી.
 - 2. ભારતના બંધારણના આમુખમાં ભારતને સાર્વભૌમ સમાજવાદી, બિનસાંપ્રદાયિક લોકશાહી દેશ બનાવવા માટે સંકલ્પ કરેલ છે.

ઉપરોક્ત વાક્યો ચકાસો.

- (A) માત્ર 1 વાક્ય યોગ્ય છે
- (B) માત્ર 2 વાક્ય યોગ્ય છે
- **(C)** 1 અને 2 બંન્ને વાક્યો યોગ્ય છે
- (D) 1 અને 2 બંન્ને વાક્યો યોગ્ય નથી
- 047. 1. મુળભૂત હક્કો જે ભાગ 3 માં દર્શાવેલ છે તે હક્કો લઈ લેતો અથવા ઓછા કરતો કાયદો રાજ્યો કરી શક્શે નહીં
 - 2. જાહેર નોકરીની બાબતમાં તકની સમાનતા આપવામાં આવેલી છે.
 - 3. અમુક દાખલામાં ઘરપકડ અને અટકાયત સામેના રક્ષણ માટે બંધારણમાં રક્ષણ આપવામાં આવેલ છે ઉપરોક્ત વાક્યો ચકાસો.
 - (A) 1, 2 અને 3 યોગ્ય છે

(B) 1 અને 2 યોગ્ય છે

(C) 2 અને 3 યોગ્ય છે

- (D) 1 અને 3 યોગ્ય છે
- 048. 1. મૂળભુત ફરજો ભાગ 4 "ક" ની કલમ 51 "ક" હેઠળ દર્શાવેલ છે
 - 2. મૂળભુત ફરજોમાં સંવિધાનનો 42મા સુધારો અને 46મા સુધારાથી બાબતો ઉમેરવામાં આવેલી છે.
 - 3. મૂળભુત ફરજો એ નૈતિક ફરજોનો ભાગ છે
 - 4. ''મૂળભુત ફરજો'' નો ખ્યાલ અમેરીકાના બંધારણમાંથી લેવામાં આવેલ છે.

ઉપરોક્ત વાક્યો ચકાસો.

(A) 1, 2 અને 4 વાક્યો યોગ્ય છે

(B) 1, 3 અને 4 વાક્યો યોગ્ય છે

(C) 1, 2 અને 3 વાક્યો યોગ્ય છે

(D) 1, 2, 3 અને 4 વાક્યો યોગ્ય છે

049.	1. રાજ્યસભામાં સભ્યપદની લાયકત માટે લઘુત્તમ ઉંમર 3	5 વર્ષની હોવી જરૂરી છે.			
	2. લોકસભામાં સભ્ય પદની લાયકાત માટે લઘુત્તમ ઉંમર 30 વર્ષની જરૂરી છે.				
	3. સંસદના સભ્યપદ માટેની લાયકાત ભારતના બંધારણની કલમ 44 માં દર્શાવેલ છે.				
	ઉપરોક્ત વાક્યો ચકાસો.				
	(A) 1 અને 3 યોગ્ય છે	(B) 2 અને 3 યોગ્ય છે			
	(C) 1 અને 2 યોગ્ય છે	D) 1, 2 અને 3 યોગ્ય નથી			
050.	નીચેના વાક્યો ચકાસો.				
	1. દરેક મંત્રીને તથા ભારતના એટર્ની જનરલને બે માંથી હક્ક છે.	કોઈ ગૃહમાં અને સંયુક્ત બેઠક હોય તો તેમાં હાજર રહેવાનો			
	2. ભારતમાં એટર્ની જનરલને, તે જે સમિતિમાં સભ્ય હો ^ર રહેતો નથી.	ય તેમાં ભાગ લેવાનો અધિકાર છે પરંતુ મત આપવાનો હક્ક			
	3. ભારતના ઉપ-રાષ્ટ્રપતિ, હોદ્દાની રૂએ લોકસભાના અધ્યક્ષ હોય છે.				
	(A) 1, 2 અને 3 વાક્યો યોગ્ય છે	(B) 2 અને 3 વાક્યો યોગ્ય છે			
	(C) 1 અને 3 વાક્યો યોગ્ય છે	D)1 અને 2 વાક્યો યોગ્ય છે			
051.	નીચેના વાક્યો ચકાસો ઃ				
	1. સભ્યપદ માટેની ગેરલાયકાતની બાબતો અંગેના પ્રશ્નો ઉ	પર નિર્ણય લેવાની સત્તા માન. રાષ્ટ્રપતિની છે.			
	2. નાણા વિધેયકો અંગેની અનુચ્છેદ 109 થી 117 ની જોગવ શકાય છે.	ાઈઓને આધીન રહીને સંસદના કોઈપણ ગૃહમાં વિધેયક લાવી			
	(A) માત્ર 1 વાક્ય યોગ્ય છે.	(B) માત્ર 2 વાક્ય યોગ્ય છે.			
	(C) 1 અને 2 બંને વાક્યો યોગ્ય નથી	D)1 અને 2 બંને વાક્યો યોગ્ય છે.			
052.	"સંસદની બેઠક ચાલુ ન હોય ત્યારે વટહુકમો પ્રસિદ્ધ કર બંધારણની કઈ કલમમાં દર્શાવેલ છે ?	વાની સત્તા માન. રાષ્ટ્રપતિને છે.'' – આ જોગવાઈ ભારતના			
	(A) 121	(B) 122			
	()123	(D) 124			
053.	1. ''રાજ્યપાલ તરીકે નિમણૂંકની શરતો અંગેની જોગવાઈ''	ભારતના બંધારણની કલમ 158માં દર્શાવેલ છે.			
	2. 'રાજ્યપાલના હોદ્દાની શરતો', ભારતના બંધારણની કલ	ન 159માં દર્શાવેલ છે.			
	ઉપરોક્ત વાક્યો ચકાસો.				
	(A) માત્ર 1 વાક્ય યોગ્ય છે.				
	(B) માત્ર 2 વાક્ય યોગ્ય છે.				
	(C) 1 અને 2 બંને વાક્યો યોગ્ય છે.				
	D) 1 અને 2 બંને વાક્યો યોગ્ય નથી.				

- 054. 1. બંધારણની કલમ 129 મુજબ, ઉચ્ચતમ ન્યાયાલય રેકોર્ડ ન્યાયાલય રહેશે.
 - 2. ફોજદારી બાબતો સંબંધી ઉચ્ચતમ ન્યાયાલયની અપીલય હકૂમત અંગેની જોગવાઈ ભારતના બંધારણની કલમ 134માં દર્શાવેલ છે.
 - 3. ઉચ્ચતમ ન્યાયાલયને રિટ કાઢવાની સત્તા ભારતના બંધારણની કલમ 139માં દર્શાવેલ છે.

ઉપરોક્ત બાબતો ચકાસોઃ

(A) 1 અને 2 યોગ્ય છે.

(B) 2 અને 3 યોગ્ય છે.

(C) 1, 2 અને 3 યોગ્ય છે.

(D) 1 અને 3 યોગ્ય છે.

- 055. નીચેના પૈકી કયું વાક્ય યોગ્ય નથી ?
 - (A) રાજ્યપાલશ્રીની નિમણુંક રાષ્ટ્રપતિ દ્વારા કરવામાં આવે છે.
 - B) સામાન્ય રીતે રાજ્યપાલશ્રીના હોદ્દાની મુદત 6 વર્ષ રહે છે.
 - (C) ભારતના બંધારણની કલમ 159 મુજબ, ઉચ્ચન્યાયાલયના મુખ્ય ન્યાયમૂર્તિ રાજ્યપાલશ્રીને પ્રતિજ્ઞા લેવડાવે છે.
 - (D) "રાજ્યપાલશ્રીને મદદ કરવા, સલાહ આપવા મંત્રી મંડળ રહેશે" આ જોગવાઈ બંધારણની કલમ 163માં કરવામાં આવેલ છે.
- 056. 1. ભારતના બંધારણની કલમ 243 ખ (243-B) મુજબ પંચાયતોની રચના કરવામાં આવે છે.
 - 2. ભારતના બંધારણના તોતેરમાં સુધારાને કારણે, આ જોગવાઈઓ બંધારણમાં દાખલ કરવામાં આવેલ છે.
 - 3. આ જોગવાઈઓ તા. 24-4-1996થી અમલમાં આવેલ છે.
 - (A) 1 અને 3 યોગ્ય છે.

(B) 1 અને 2 યોગ્ય છે.

(C) 2 અને 3 યોગ્ય છે.

- (D) 1, 2 અને 3 યોગ્ય છે.
- 057. 17 SDGs (Sustainable Development Goals) ની સિદ્ધિમાં સને 2020ના નીતિ આયોગ મુજબ પ્રથમ અને બીજા સ્થાને કયા રાજ્યો છે ?
 - \Lambda કેરળા અને હિમાચલ પ્રદેશ

(B) કેરળા અને તામિલનાડુ

(C) હિમાચલ પ્રદેશ અને ગોવા

- (D) તામિલનાડુ અને ગોવા
- 058. North Eastern Region District SDG Index કોના દ્વારા જાહેર કરવામાં આવેલ છે ?
 - (A) રીઝર્વ બેન્ક ઑફ ઈન્ડીયા

(B) નાબાર્ડ

(C)નીતિ આયોગ

(D) નાણા મંત્રાલય

059. યોગ્ય જોડકા જોડો.

વિગત ભારતના બંધારણની કલમ

- 1. સંઘ અને રાજ્યોના લોકસેવા આયોગ
- a. 320

2. લોક સેવા આયોગના કાર્યો

b. 323

3. સભ્યોની નિમણૂંક-મુદત

c. 315

4. લોક સેવા આયોગના રીપોર્ટ (A) 1 - a, 2 - d, 3 - b, 4 - c

d. 316

(B) 1 - c, 2 - a, 3 - d, 4 - b

(C) 1 - d, 2 - b, 3 - c, 4 - a

(D) 1 - b, 2 - c, 3 - a, 4 - d

10

060.	?ના ૧	જગ્યા પુ	રાં.												
	(A) 7	7	2	3	11		5	5		8	1				
	(B) 8 (C) 9											_			
	(D) 10	9	4	6	2		6	6		4	?				
061.	?ની '	જગ્યા પુ	રો. 🦯	9 (8) (4									
	(A) 12				✓										
	(B) 14			2											
	(C) 16			8 (16		?									
	(D) 18			•		\mathcal{L}									
062.	?ની વ	જગ્યા પુ	રો.		_										
	(A) M			F		1)	\setminus		>						
	(B) N		A	$\mathbf{K} \setminus \mathbf{K}$	D	P) (B	?							
	(C) O			1		2		$\frac{\downarrow}{3}$							
	(D) P			1											
063.			9, 44, 5	51,,	., 1	<u>નાલી</u>	જગ્યા								
	(A) 58, 6							, ,		66, 73					
	(C) 56, 6		_							61, 69		_			
064.	78 કિમી/ક કેટલી હશે		જડપે જ	૪તી ટ્રેનની ^૯	તુંબાઇ <u>(</u>	800 ¥	ીટર છે) અને ત	ો એક	: ટનલ	1 મીની	.ટમાં પસાર	કરે છે તે ટ	:નલની લ <u>ં</u>	બાઇ
	(A) 400 °	મીટર						(B)	500	મીટર					
	(C) 600 ³	મીટર						(D)	700	મીટર					
065.	એક વેપાર્ર	ોને ખરીય	દ કિંમત	ા ઉપર 22 $\frac{1}{2}$	% નફ	ો મેળ	વવો છે	. જો તે ન	ો વેચ	ાણ રૂા.	39200	હોય તો તે	ને કેટલો નફ	ો મળેલ હ	ડશે ?
	(A) રૂા. 5									5,400					
	(C) રૂા. 7	,200						(D)	રૂા. ક	8,000					
066.	એક ચુંટર્ણ ટકા (%)			યારોને અનુક ?	કમે 113	36, 76	636 અ	ને 11,6	528 1	ાત મળ	યાં, આ	સંજોગોમાં	જીતેલા ઉમે	ોદવારને કે	કેટલા
	(A) 57%)						(B)	54%	o O					
	(C) 47%)						(D)	67%	o					
067.		. •		ાજન 45 કી ાાં B નું વજ			_	તરેરાશ	વજન	ા 40 કી	લો છે ચ	બને B અને	C નુ વજન	સરેરાશ વ	વજન
	(A) 38 £			J	·			(B)	34 \$	ોલો					
	(C) 31 s							, ,	27 5						
															_

oxide

(C) સિલિકોન ડાયોકસાઈડ અને જર્મેનિયમ ઓક્સાઈડનું મિશ્રણ (mixture of Silicon dioxide and Germanium

076.	વૉશીંગ સોડા (washing soda) નું સામાન્ય	નામ :				
	A) સોડીયમ કાર્બોનેટ (Sodium carbonate)					
	(B) કેલ્શીયમ કાર્બાઇડ (Calcium carbide)					
	(C) કેલ્શીયમ બાયકાર્બોનેટ (Calcium bicarbonate)					
	(D) સોડીયમ બાયકાર્બોનેટ (Sodium bicarbonate)					
077.	"ટેટ્રાએથિલ લીડ" (Tetraethy lead) નો	શું ઉપયોગ થાય છે ?				
	(A) દુઃખ/પેન ઘટાડવા (painkiller)					
	(B) આગ બુજાવવા (fire extinguisher)					
	(C) મચ્છર મારવાની દવા તરીકે (mosquito repellent)					
	D) પેટ્રોલમાં ઉમેરણ (petrol additive)					
078.	ભારત અને યુ.કે. (U.K.) ના વૈજ્ઞાનિકોએ ''	'Hand washing robot'' બનાવેલ છે તેનુ શું નામ આપેલ છે.				
	(A) ગોપી (Gope)	(B) હેપી (Hepe)				
	(C) હોપ (Hope)	D) પેપી (Pepe)				
079.	ભારતમાં એટોમીક એનર્જી 'Atomic ener	gy' ના પિતા કોને ગણવામાં આવે છે ?				
	(A) એ.પી.જે. અબ્દુલ કલામ (A.P.J. Abdul Kalam)					
	B) હોમી જે. ભાભા (Homi J. Bhabha)					
	(C) રાજા રમન્ના (Raja Ramanna)					
	(D) હોમી સેઠના (Homi Sethna)					
080.	એડીક્ટીવ મેન્યુફેક્ચરીંગ (addictive mar	nufacturing) ને બીજા કયા નામથી પણ ઓળખવામાં આવે છે ?				
	(A) 2-D પ્રીન્ટીંગ (2-D printing)					
	(B) 3-D પ્રીન્ટીંગ (3-D printing)					
	(C) CPU એસમ્બલી (CPU assembly)					
	(D) મેમરી મેનેજમેન્ટ (memory manage	ement)				
081.	નીચેના પૈકી કોને "ઈન્કલેસ પ્રિન્ટર" (inkl	ess printer) તરીકે પણ ઓળખવામાં આવે છે ?				
	(A) થર્મલ પ્રિન્ટર (thermal printer)					
	(B) ઈન્ક જેટ પ્રિન્ટર (inkjet printer)					
	(C) OCR					
	(D) ડૉટ મેટ્રીક્સ પ્રિન્ટર (dot matrix pri	nter)				
082.	એનવીરોનમેન્ટ (environment) શબ્દ કઈ	ભાષામાંથી લેવામાં આવેલ છે ?				
	(A) ગ્રીક	(B) સ્પેનીશ				
	(C) અંગ્રેજી	(D) ફેન્ચ				

090. દિલ્હી-મુંબઈ હાયવે કે જે ભારતનો સૌથી લાંબો એક્સપ્રેસ હાયવે છે, તે કેટલા રાજ્યોમાંથી પસાર થાય છે ?

(A) 4

(B) 5

(C) 6

(D) 7

091. ઓસ્ટ્રેલીયા દ્વારા કયા દેશોના સહકારથી "ન્યુક્લીયર - પાવર" સંચાલીત સબમરીન બનાવવાનાં કરારો કરેલ છે ?

(A) ફ્રાન્સ અને જર્મની

(B) બ્રીટન અને ફ્રાન્સ

(C) ભારત અને અમેરીકા

(D) બ્રીટન અને અમેરીકા

092.	વર્લ્ડ પેશંટ સેફ્ટી ડે (World Patient Safety Day) ક્યા	રે ઉજવાય છે ?
	(A) 15 સપ્ટેમ્બર	(B) 16 સપ્ટેમ્બર
	(C) 17 સપ્ટેમ્બર	(D) 18 સપ્ટેમ્બર
093.	NCC ની વ્યાપક સમીક્ષા કરવા સંરક્ષણ મંત્રાલય દ્વારા કોન	ા અધ્યક્ષ સ્થાને કમીટી રચવામાં આવેલ છે ?
	(A) આનંદ મહીન્દ્રા (Anand Mahindra)	(B) બાયજયંત પાંડા (Baijayant Panda)
	(C) એમ.એસ. ધોની (M.S. Dhoni)	(D) વસુધા કામત (Vasudha Kamat)
094.	AI based ભાષાના અનુવાદ માટેનું સોફ્ટવેર-પ્રોજેક્ટ ઉડ	ાન કઈ સંસ્થા દ્વારા વીકસાવેલ છે ?
	(A) IIT, Delhi	(B) IIT, Mumbai
	(C) IIT, Kanpur	(D) IIT, Chennai
095.	બ્લાસ્ટ ફરનેસ (Blast Furnace) માંથી બારોબાર C વિકસાવેલ છે ?	$\mathbf{O_2}$ ખેંચી શકે તેવું ભારતનું પ્રથમ $\mathbf{CO_2}$ કેપ્ચર પ્લાન્ટ કોણે
	(A) L&T	(B) ONGC
	C) Tata Steel	(D) BHEL
096.	લશીથ મલીન્ગા (Lashith Malinga) કે જેઓએ હાલમાં	ક્રિકેટમાંથી નિવૃત્તી લીધેલ છે તેઓ કયા દેશના ખેલાડી હતા ?
	(A) વેસ્ટ ઈન્ડીઝ (West Indies)	(B) બાંગ્લાદેશ (Bangladesh)
	(C) ઈંગ્લેન્ડ (U.K.)	D) શ્રીલંકા (Sri Lanka)
097.	પીસફુલ મીશન 2021 "Peaceful Mission 2021" એક ભાગ લીધેલ હતો ?	ક્સરસાઈઝ કયા દેશ દ્વારા યોજવામાં આવેલ હતી જેમા ભારતે
	(A) રશિયા	(B) ઓસ્ટ્રેલીયા
	(C) ચીન	(D) બાં ^{ગ્} લાદેશ
098.	ઝીરો પોલ્યુશન ડીલીવરી વાહનો માટે કઈ સંસ્થા દ્વારા કેમ્પે	ન શૂન્ય (Campaign Shoonya) શરૂ કરવામાં આવેલ છે ?
	(A) ઈસરો	B) નીતિ આયોગ
	(C) IIT, ચેન્નર્ઇ	(D) કેનેરા બેન્ક
099.	"રાજા મહેન્દ્રપ્રતાપ સીંઘ યુનિવર્સિટી"નો શીલાન્યાસ માન.	વડાપ્રધાન દ્વારા કયા શહેરમાં કરવામાં આવેલ હતો ?
	(A) મેરઠ	(B) વારાણસી
	() અલીગઢ	(D) જયપુર
100.	કીંગ શેજોગ લીટરસી પ્રાઈઝ-2021 (King Sejong Liter આવે છે. તે કઈ સંસ્થાને આપવામાં આવેલ છે ?	acy Prize-2021) કે જે યુનેસ્કો (UNESCO) દ્વારા આપવામાં
	(A) IGNOU	(B) CBSE
	(C) NCERT	(D) NIOS

- 101. The value of the temperture co-efficient of material depends on
 - (A) length of the material

(B) cross sectional area of the material


(C) volume of the material

- (D) nature of the material and temperature
- 102. Two electric bulbs rated for the same voltage have powers of 200 W and 100 W respectively. If their resistances are respectively R, and R,, then
 - (A) $R_1 = 2R_2$

(B) $R_2 = 2R_1$

(C) $R_{1} = 4R_{1}$

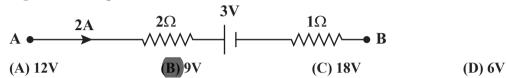- (D) $R_1 = 4R_2$
- 103. Figure shows a part of closed circuit. What is the value of VA VB?



- 104. A house is served by a 220V line. In a circuit protected by a fuse marked 9A, the maximum number of 60W lamps (operating at unity pf) in parallel that can be turned on is
 - (A) 33

(B) 44

(C) 22

- (D) 20
- 105. A circuit consisting of inductance L = 10H and $R = 2 \Omega$ is switched on to a dc supply of 20V. The time taken by the current to reach 63.2% of its final value is
 - (A) 20 sec

(B) 10 sec

(C) 5 sec

- (D) 2 sec
- 106. A certain air capacitor has a capacitance of 20 μ F. If a dielectric having relative permittivity of 5 is introduced between the plates, the value of capacitance would be
 - (A) 100 μF

 $(B) 4 \mu F$

(C) 20 µF

- (D) $0.25 \mu F$
- 107. In a certain RLC series circuit fed from an AC source, the value of power factor at resonance is
 - (A) unity
 - (B) zero lagging
 - (C) zero leading
 - (D) zero leading or zero lagging depending upon the value of inductor and capacitor
- 108. A balanced star connected load having an impedance of Z/ϕ and connected to a 3- ϕ source may be replaced by an equivalent delta connected load having an impedance of
 - (A) Z/φ

(B) $\mathbb{Z}/3\varphi$

(C) $0.33Z/\phi$

- (D) $3Z/\varphi$
- 109. If the separation between the three phases of a transmission system is increased
 - (A) the inductance will increase and capacitance will remain unchanged
 - (B) both the inductance and capacitance will decrease
 - (C) the inductance will increase and capacitance will decrease
 - (D) both the inductance and capacitance will increase




- 110. A certain periodic voltage waveform has an rms value = 30V, average value = 20V and peak value = 60V. Its form factor is
 - (A) 1.5

(B) 2

(C)3

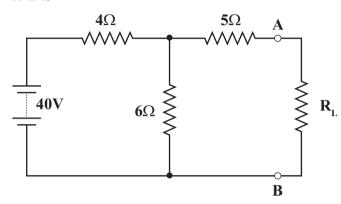- (D) 0.66
- 111. For the circuit shown in figure the value of Thevenin equivalent resistance Rth across terminals A-B is



(A) 15Ω

(B) 3.5Ω

(C) 6.4Ω

- (\mathbf{D}) 7.4 Ω
- 112. According to maximum power transfer theorem, under the conditions of maximum power transfer, the efficiency is
 - (A) 75%

(B) 100%

(C) 50%

- (D) 25%
- 113. In a two-port network containing linear, bilateral passive circuit elements, which one of the following conditions for z-parameters would hold?
 - (A) $z_{11} = z_{22}$

(B) $\mathbf{z}_{11}\mathbf{z}_{21} = \mathbf{z}_{11}\mathbf{z}_{22}$

(C) $\mathbf{z}_{11}\mathbf{z}_{12} = \mathbf{z}_{22}\mathbf{z}_{21}$

- (D) $z_{12} = z_{21}$
- 114. In a two-port network, the output short circuit current was measured while the source voltage at the input was 1V, the value of the output current would provide the parameter
 - (A) C

(B) y_{12}

 $(C) h_{21}$

- $\mathbf{D}\mathbf{y}_{21}$
- 115. $s/(s^2 + \omega^2)$ is the Laplace transform of
 - (A) sinot

(B) coswt

(C) coshot

- (D) sinhot
- 116. For V(s) = (s + 2)/(s(s + 1)), the initial and final values of v(t) will be respectively
 - (A) 1 and 1

(B) 2 and 2

(C) 2 and 1

(D) 1 and 2

[BBE]

[P.T.O.

(D) 18°

 $(C) 72^{\circ}$

	[BBE		[P.T.O. 19		
	(D) rotates at synchronous speed with respect to	to rotor			
	(C) rotates at slip speed with respect to stator				
	(B) is standstill with respect to stator mmf				
	(A) rotates at the speed of rotor in the air gap				
134.	The mmf produced by the current of 3-f induc	tion motor			
	(C) its power factor will reduce	(D) its breakdown torque will redu	ice		
	(A) its speed will reduce	(B) its efficiency will improve			
133.	In an induction motor, if the air gap is increase				
122	•	` '			
	(C) normally excited	(D) disconnected from the common	n terminals		
	(A) underexcited	(B) overexcited			
132.	An induction motor and synchronous motor are connected to a common feeder line. To operate the feeder line at unity pf, the synchronous motor should be				
	(D) rotor speed exceeds the synchronous speed				
	(C) rotor speed falls below the synchronous speed.				
	(B) rotor speed is equal to synchronous speed				
	(A) rotor speed either exceeds or falls below th	e synchronous speed			
131.	In a synchronous motor, the synchronizing pov				
121					
	(C) lagging and the current will increase (D) leading and the current will increase				
	(C) lagging and the current will decrease				
	(B) lagging and the current will increase				
	(A) leading and the current will decrease				
130.	A synchronous motor is operating on no-load at the power factor will become	unity power factor. If the field currei	it is increased,		
130					
	(C) X'd > X''d > Xd	(D) $X d > X' d > X' d$ (D) $X d > X'' d > X' d$			
	(A) $Xd > X'd > X''d$	(B) $X''d > X'd > Xd$			
129.	If Xd, X'd and X''d are the steady state, to synchronous machine respectively, which of th		eactance of a		
	C) EMF method	(D) ASA method			
	(A) ZPF method	(B) MMF method			
	an alternator?	(D) MME mathed			
128.	Which one of the following methods would give	e higher than actual value of voltage	e regulation of		
	(D) reactance either due to armature reaction	or leakage flux			
	(B) reactance due to leakage flux				
	(A) reactance due to armature reaction of the machine				

127. The synchronous reactance is the

IVI		
135.	A 4-pole, 50 Hz induction motor runs current is	at a speed of 1440 rpm. The frequency of the rotor
	(A) 3 Hz	(B) 2.5 Hz
	(C) 1 Hz	(D) 2 Hz
136.	Candela is the unit of which of the follow	ving?
	(A) Wavelength	B) Luminous intensity
	(C) Luminous flux	(D) Frequency
137.	An induction motor when started on 1/7th of rated speed. The motor is said to	load does not accelerate upto full speed but runs at
	(A) locking	(B) plugging
	(C) crawling	(D) cogging
138.	In a single phase shaded pole squirrel ca (A) leads the flux in the unshaded pole so	ge induction motor, the flux in the shaded part always
	(B) is in phase with the flux in the unshad	ded pole segment
	(C) lags the flux in the unshaded pole seg	gment
	(D) is 180 out of phase with the unshaded	d pole segment
139.	A universal motor runs at	
	A) higher speed with dc supply and with	ı less sparking
	(B) higher speed with ac supply and with	less sparking
	(C) same speed with ac and dc supply	
	(D) higher speed with ac supply but with	increased sparking at the brushes
140.	An over current relay used for phase to j	phase fault protection can be set at
	(A) 20% to 200 % of the rated current in	steps of 10%
	(B) 10% to $100~\%$ of the rated current in	steps of 10 %
	(C) 10% to 50 % of the rated current in	steps of 5 %
	D)50% to 200 % of the rated current in	steps of 25 %
141.	In a 4-pole, 25 kW, 200V wave wound dc	shunt generator, the current in each parallel path will be
	A) 62.5 A	(B) 125 A
	(C) 31.25 A	(D) 250 A
142.	If the applied voltage is 230V, then the ba	ack emf, for maximum power developed is
	(A) 115 V	(B) 200 V
	(C) 230 V	(D) 460 V

143.	The speed of a dc shunt motor is				
	(A) directly proportional to back emf and flux				
	(B) directly proportional to back emf and inversely proportional to flux				
	(C) inversely proportional to both back emf and flux				
	(D) directly proportional to flux and inversely p	proportional to back emf			
144.	A dc shunt motor, running lightly at 1000 rpm is operated under plugging. With pluconnections left as it is, the final speed of the motor will be				
	(A) zero	(B) 1000 rpm			
	(C) slightly less than 1000 rpm	D) 1000 rpm in reverse direction			
145.	If the field circuit of a dc shunt generator excee	ds its critical value, the generator			
	A) fails to build up	(B) builds up a very high voltage			
	(C) exceeds its current capacity	(D) produces power beyond its rating			
146.	Open circuit test on a transformer gives				
	(A) hysteresis loss	(B) eddy current loss			
	(C) copper loss	D) sum of hysteresis and eddy current loss			
147.	A 10 kVA, 400/200 V single phase transformer circuit line current of	with 10% impedance draws a steady state short			
	(A) 50 A	(B) 150 A			
	(C) 250 A	(D) 350 A			
148.	Two coupled coils connected in series have an econ their connection. The mutual inductance M	quivalent inductance of 16 mH or 8 mH depending between the coils is			
	(A) 2 mH	(B) 4 mH			
	(C) 12 mH	(D) 8√2 mH			
149.	A dc shunt motor has external resistance of Ra ar The armature current at starting can be reduced	nd Rf in the armature and field circuits respectively.			
	(A) Rf maximum and Ra minimum	(B) Ra maximum and Rf maximum			
	(C) Ra minimum and Rf maximum	(D) Ra maximum and Rf minimum			
150.	*	are supplied from the same source. One of the onnection. The phase difference between the two s would be			
	(A) 0 degree	(B) 30 degrees			
	C) 60 degrees	(D) 120 degrees			
151.	The inductance of line is minimum when				
	(A) GMD is high	(B) GMD is high and GMR is low			
	(C) both GMD and GMR are high	D)GMD is low and GMR is high			

М					
152.	Which of the following power plants w load operation?	vill take least time in starting from cold conditions to full			
	(A) Nuclear power plant	(B) Steam power plant			
	C) Hydroelectric plant	(D) Gas turbine power plant			
153.	Shunt capacitance is usually neglected A) short transmission lines (B) medium transmission lines (C) long transmission lines (D) medium and long transmission line	·			
154.	•	gible resistance and capacitance has an inductive reactance and inductive reactance and receiving-end voltages are maintained at the transmitted is			
	(A) 121 MW	(B) 121√3 MW			
	(C) 363 MW	(D) 363 kW			
155.	Series compensation on EHV lines is re (A) reduce the fault level (B) improve the stability (C) improve the voltage profile (D) as a substitute for synchronous pha				
156.	If the penalty factor of a plant is unity,	its incremental transmission loss is			
	(A) 1.0	(B) - 1.0			
	(C) Zero	(D) Infinity			
157.	A transmission line of 210 km length ha then the parameter	s certain values of A, B, C, D. If the length is made 100 km			
	(A) A increases and B decreases	(B) A and B both decrease			
	(C) A and B both increase	(D) A decreases and B increases			
158.	For protection of parallel feeders fed fr	om one end, the relays required are			
	(A) Non-directional relays at the source end and directional relays at the load end (B) Non-directional relays at both the ends				
	(C) Directional relays at the source end(D) Directional relays at both the ends	and non-directionals relays at the load end			
159.	In GS method of load flow, a voltage cowhen	ntrolled bus is treated as a load bus in subsequent iteration			
	(A) active power limited is violated	(B) reactive power limit is violated			

(D) phase angle limit is violated

(C) voltage limit is violated

160.	The unit protection scheme provides				
	(A) primary protection	(B) back-up protection			
	(C) simultaneous protection	(D) remote protection			
161.	Mho relay is normally used for the protection of				
	A)Long transmission lines	(B) Medium length lines			
	(C) Short length lines	(D) No length criterion			
162.	The velocity of travelling wave through a cable	of relative permittivity of 9 is			
	(A) 9×10^8 metres/sec	(B) 3×10^8 metres/sec			
	C)10 ⁸ metres/sec	(D) 2×10^8 metres/sec			
163.	Which of the following statements is correct from	om power system stability point of view?			
	(A) The higher the initial load, the larger the cr	ritical clearing angle			
	B) The higher the initial load, the lower the cri	tical clearing angle			
	(C) The initial load has nothing to do with criti	cal clearing angle			
	(D) The higher the operating time of the clearing angle	circuit breaker, the larger will be the critical			
164.	For a load flow solution, the quantities specified at the load bus are				
	A)P and Q	(B) P and $ V $			
	(C) Q and $ V $	(D) P and load angle δ			
165.	•	is connected to an infinite bus having a voltage of alterator reactance is 0.2 pu, the maximum power			
	(A) 8 pu	(B) 2 pu			
	(C) 2.67 pu	(D) 5 pu			
166.	The inrush current of a transformer at no load	is maximum if the supply voltage is switched on			
	A) at zero voltage value	(B) at peak voltage value			
	(C) at V/2 value	(D) at $\sqrt{3}/2$ V value			
167.	The insulation resistance of a cable of length 1 insulation resistance will be	$10~\mathrm{km}$ is $1~\mathrm{M}\Omega.$ For a cable of length $100~\mathrm{km},$ the			
	(A) $10 \text{ M}\Omega$	(B) 5 MΩ			
	C)0.1 MΩ	(D) 20 MΩ			
168.	If positive, negative and zero sequence networ connected in parallel, the type of fault that has	ks for a particular fault on the power system are occurred is			
	(A) single line to ground fault	B) double line to ground fault			
	(C) line to line fault	(D) open circuit			

IVI				
169.	The voltages across the various discs of a string of suspension insulators having identical discs are different due to			
	(A) surface leakage currents	(B) series capacitance		
	C) shunt capacitance to ground	(D) series and shunt capacitances		
170.	Four identical alternators each rated for 20 are working in parallel. The short circuit le	MVA, 11 kV having a subtransient reactance of 16% wel at the bus-bars is		
	(A) 500 MVA	(B) 400 MVA		
	(C) 125 MVA	(D) 80 MVA		
171.	A string insulator has 4 units. The voltage across the bottom-most unit is 33.33% of the tota voltage. Its string efficiency is			
	(A) 25%	(B) 33.33%		
	(C) 66.67%	(D) 75%		
172.	A wave-trap is used at the termination of a	HVAC overhead line to a station switchyard to		
	(A) prevent the transformer magnetising ha	(A) prevent the transformer magnetising harmonics from reaching the overhead line		
	(B) damp the incoming surge waves from the overhead line			
	(C) attenuate sub-harmonic oscillations			
	D) provide for carrier communication			
173.	In which one of the following models of transmission lines, is the full charging current assumed to flow over half the length of the line only?			
	(A) Equivalent - π	(B) Short line		
	(C) Nominal - π	(D) Nominal-T		
174.	The percentage differential protection of a	transformer protects the transformer against		
	(A) external faults	(B) internal faults		
	(C) magnetising current inrush	(D) overloading		
175.	The boundary of a protective system is determined by the location of			
	(A) circuit breakers	(B) transformer		
	C)CTs	(D) PTs		
176.	For the protection of stator winding of an alternator against internal faults involving ground, the relay used is a			
	A) biased differential relay	(B) directional overcurrent relay		
	(C) plain impedance relay	(D) Buchholz relay		
177.	For the protection of a large squirrel cage i	nduction motor against single phase, normally		
	(A) an over current relay is used	(B) a differential relay is used		
	(C) a directional relay is used	(D) negative sequence current relay is used		



		[BBE]	P.T.O. 25
	(C) 120	(D) 180	
	(A) 0	B) 90	
186.	In an electrostatic field, the ansurface is	gle between electric field intensity vector and	equipotential
107	(C) undefined	(D) zero	
	(A) unity	(B) negative	
185.	The divergence of curl of magnetic	·	
10=	$(C)D_{N} = \rho_{s}$	$(D) D_{N} = 0$	
	$(A) D_t = \rho_v$	$(B) D_t = \rho_s$	
184.	and D_N represent tangential and n volume charge density)	is correct for conductor-dielectric boundary conditions to the component of electric flux density 'D', while	
	(C) $\nabla^2 V = J$	(D) $\nabla^2 \mathbf{V} = \boldsymbol{\rho}_s$	
	$(A)\nabla^2 V = 0$	(B) $\nabla^2 V = E$	
183.	- 3	d intensity, electric potential, current density and su f the following gives Laplacian equation?	ırface charge
	(C) Electric flux density	(D) Magnetic field intensity	
	(A) Magnetic flux density	B) Volume charge density	
182.	Which of the following is not a vec	ctor quantity?	
	(C) 5 N	(D) 2.5 N	
	(A) 20 N	(B) 10 N	
181.		arged particles, separated by a distance of 3 m is nes 6 m, then according to Coulomb's law the force b	
	(D) breaking the circuit under ove	erload condition	
	C) breaking the circuit under no	load condition	
	(B) making under fault conditions	s	
	(A) breaking abnormal current		
180.	An isolator is meant for		
	(C) minimum oil circuit breakers	(D) air blast circuit breakers	
	(A) all breakers	(B) bulk oil circuit breakers	
179.	Resistance switching is normally e	employed in	
	(C) fifth harmonic current	(D) seventh harmonic current	
	(A) second harmonic current	(B) third harmonic current	
	relay restraining coil is biased with	h	

178. To prevent mal-operation of differentially connected relay while energising a transformer, the

IVI

26		[BBE]	[Contd.
	(D) none of the above	_	
	(C) torque and speed both are proportional to the square of the armature current		
	B) torque is proportional to the square of t to the torque	the armature current and speed is inversely pro	oportional
	(A) torque is proportional to the square of torque	f the armature current and speed is proportion	onal to the
194.	DC series motors are best suited for tracti	on because	
	(C) load current	(D) load voltage	
193.	The primary current in a current transfor (A) the secondary burden	mer is dictated by (B) the core of the transformer	
102			
	(A) $\theta e = (2/P)\theta m$ (C) $\theta e = \theta m$	(B) $\theta e = p\theta m$ (D) $\theta e = (P/2)\theta m$	
192.	given by	n electrical angle θ e and mechanical angle θ m	degrees is
	(C) China	D) New Zealand	
	(A) USA	(B) Canada	
191.	Electricity distribution company named Powerco, will be testing long distance wireless power transmission technology developed by a start-up called Emrod in		
	(D) two surface inegrals		
	C) surface integral and volume integral		
	(B) line integral and volume integral		
	(A) line integral and surface integral		
190.	The divergence theorem gives relationship	between	
	(C) 5 kV/m	(D) 40 kV/m	
	the plane would be (A) 10 kV/m	B) 20 kV/m	
189.	·	ite sheet charge at a point 4 m from the plane $20~\mathrm{kV/m}$. The electric field intensity at a point	
	(C) $\delta I/dt$	(D) δV/dt	
	equation $\nabla \times \mathbf{H} = \mathbf{J}$, for time varying fields (A) $\delta \mathbf{D}/dt$	(B) δB/dt	,
188.	According to Maxwell, which term is add	ditionally required to be considered (i.e. add	ed) in the
	(C) Poisson's theorem	(D) Gaussian theorem	
107.	A) Stoke's theorem	(B) Divergence theorem	
187.	If H represents magnetic field intensity, th	en $\phi H.dL = \int (\nabla \times H).dS$ represents	



195.	A voltage waveform $V(t)=12t^2$ is applied across a 1H inductor for $t\geq 0$, with initial current through it being zero. The current through the inductor for $t\geq 0$ is given by		
	$(A) 4t^3$	(B) 12t	
	(C) 24t	(D) $12t^3$	
196.	o c	W and 60W having same voltage rating are connected in series e following statement is necessarily true?	
	(A) the bulbs together consume 100) W	
	(B) the bulbs together consume 50	W	
	(C) the 60W bulb glows more brighter		
	(D) the 40W bulb glows more brigh	nter	
197.	·	ator is feeding a partly inductive load. A capacitor is now etely nullify the inductive current. For this operating condition	
	(A) the field current and fuel input	have to be reduced	
	(B) the field current and fuel input have to be increased		
	(C) the field current has to be incre	ased and fuel input left unaltered	
	(D) the field current has to be reduced and fuel input left unaltered		
198.	A synchronous generator is feeding a zero power factor (lagging) load at rated current. The armature current is		
	(A) magnetizing	B) demagnetizing	
	(C) cross magnetizing	(D) ineffective	
199.	Two capacitors of capacitances 2 pF and 6 pF are connected in parallel across a 120V dc source. The sum of total charges on the capacitors is		
	(A) 15 pC	(B) 1980 pC	
	(C) 180 pC	D) 960 pC	
200.	A double circuit line running between Vindhyachal and Varanasi which was recently commissioned in July 2021 has a transmission voltage of		
	(A) 400 kV	(B) 500 kV	
	(C) 765 kV	(D) 1200 kV	
201.	The digital multiplexer is basically a combinational logic circuit to perform the operation		
	(A) AND - AND	(B) OR - OR	
	C)AND - OR	(D) OR - AND	
202.	Which semiconductor power device out of the following is not a current triggered device?		
	(A) Thyristor	(B) G.T.O.	
		D) MOSFET	

(B) Gujarat Electricity Regional Commission(C) Gujarat Electricity Regulatory Committee(D) Gujarat Electricity Regulatory Commission

212.	212. In a sequenctial circuit, the outputs at any instant of time depends	
	(A) only on the inputs present at that instant of time	
	B) on past outputs as well as present inputs	
	(C) only on the past inputs	
	(D) only on the present outputs	
213.	The TRIAC can be used only in	
	(A) Inverter	(B) Rectifier
	(C) Multiquadrant Chopper	(D) Cycloconverter
214.	A trigonometric Fourier series of a peridoic fur	nction can have only
	(A) cosine terms	(B) sine terms
	(C) cosine and sine terms both	(D) D.C. and cosine terms
215.	In position control systems, the device used for	providing rate feedback voltage is called
	(A) Potentiometer	(B) Synchro Transmitter
	(C) Synchro Transformer	(D) Tachogenerator
216.	Which of the following interrupts are unmaska	able interrupts?
	(A) RST 5.5	(B) RST 7.5
	CTRAP	(D) INTR
217.	A d.c. motor runs at 1725 rpm at full load and	1775 rpm at no load. The speed regulation is
	(A) 4.7%	(B) 2.9%
	(C) 7.6%	(D) 1.5%
218.	Under the conditions of maximum power trans	sfer, a voltage source is delivering a power of 30 W
	to the load. The power generated by the source	
	(A) 45 W	(B) 30 W
	(C) 60 W	(D) 90 W
219.		00 W, 220 V and 1000 W, 220 V respectively. The
	resistance of the heater is	
	(A) More than that of the fan	(B) Less than that of the fan
	(C) Equal to that of the fan	(D) Zero
220. Non-contact flow measurement can be carried out by		out by
	(A) Orifice meter	(B) Turbine flow meter
	(C) Ultrasonic flow meter	(D) Magnetic flow meter
221.	Coolant used in thyristor/IGBT valves is	
	(A)Air	(B) SF6

M		
222.	What is full form of GEDA? (A) Gujarat Energy Development Association (B) Gujarat Electricity Development Association (C) Gujarat Energy Development Agency (D) Gujarat Electrical Development Agency	n
223.	The first HVDC scheme in INDIA is (A) Vidhyachal back-to-back System (C) Delhi-Rihand 500KV system	(B) Chadrapur-Padghe Scheme (D) Sileru-Barsoor System
224.	The output of a 2-input OR gate is 0 only when (A) Both inputs are 0 (C) Both inputs are 1	it's (B) Either input is 1 (D) Either input is 0
225.	How many select lines would be required for an (A) 2 (C) 8	8-line-to-1-line multiplexer? (B) 4 (D) 3
226.	A converts a fixed voltage DC source in (A) Inverter (C) Chopper	nto a variable voltage DC source. (B) Rectifier (D) Cycloconverter
227.	A TRIAC is (C) 2 terminal switch	(B) 3 terminal unidirectional switch(D) 2 terminal bilateral switch
228.	Graphical representation of a signal in time dor (A) Frequency System (C) Waveform	nain is called (B) Frequency (D) None of the above
229.	A cumulatively compounded motor does not rupresence of (A) shunt winding (C) interpoles	n at dangerous speed at light loads because of the (B) series winding (D) compensating windings
230.	Which of the following logic family is fastest of (A) TTL (C) DCTL	all? (B) RTL (D) ECL
231.	In force voltage analogy, velocity is analogous to (C) Inductance	(B) Charge (D) Capacitance

232.	The type 0 system has at the origin.	
	A)no pole	(B) net pole
	(C) simple pole	(D) two pole
233.	In a single-phase half wave inverter,	SCR(s) is/are gated at a time.
	(A) one	(B) two
	(C) three	(D) four
234.	The output of a single-phase half bridge inver-	ter on R load is ideally
	(A) A sine wave	(B) A cosine wave
	C) A square wave	(D) A constant DC
235.	In an inverse definite time electromagnetic achieved because of	over current relay, the minimum time feature is
	A) saturation of the magnetic circuit	(B) proper mechanical design
	(C) appropriate time delay element	(D) electromagnetic damping
236.	HVDC transmission is mainly used for	
	A) bulk power transmission over very long di	stance
	(B) inter connecting two systems with the same	e nominal frequency
	(C) eliminating reactive power requirement in	the operation
	(D) minimizing harmonics at the converter sta	tions
237.	The origin for the investigation of closed loop stability in relation to Nyquist criterion is	
	(A) - 1 + j0	(B)+1+j0
	(C) 0 + j1	(D) $0 - j1$
238.	The initial slope of the bode plot gives an indic	eation of the
	A) type of system	(B) nature of the system time response
	(C) system stability	(D) gain margin
239.	The decimal equivalent of the hexadecimal number E5 is	
	(A) 279	B) 229
	(C) 427	(D) 3000
240.	In a microprocessor, the resistor which holds t	he address of the next instruction to be fetched is
	(A) Accumulator	B) Program Counter
	(C) Stack Pointer	(D) Instruction Register
241.	If the fault current is 2000A, the relay plug set setting multiplier will be	ting is 50% and the CT ratio is 200/5, then the plug
	(A) 25	B) 20
	(C) 50	(D) 45

242. In a d.c. generator, the armature reaction (A) weakens the flux at the trailing pole tip (B) weakens the flux at the leading pole tip (C) strengthens the flux at the leading pole tip (D) none of the above 243. What is full form of THD in the context of inverter output waveform? (A) Total Harmonic Disorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Disorder (E) Rectifier (C) Chopper (D) Cycloconverter 244. A converts a fixed voltage DC source into a AC source. (A) Inverter (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (B) demultiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) he halved (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/matt	M		
B) weakens the flux at the leading pole tip (C) strengthens the flux at the leading pole tip (D) none of the above 243. What is full form of THD in the context of inverter output waveform? (A) Total Harmonic Distorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Distorder 4 converts a fixed voltage DC source into a AC source. A) Inverter (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit (C) be doubled (D) be quadrupled 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (D) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/math	242.	In a d.c. generator, the armature reaction	
(C) strengthens the flux at the leading pole tip (D) none of the above 243. What is full form of THD in the context of inverter output waveform? (A) Total Harmonic Disorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Disorder (E) Total Harmonic Distortion (D) Theoretical Harmonic Disorder 244. A converts a fixed voltage DC source into a AC source. (A) Inverter (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (T) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt (D) 2.5 lumen/watt		(A) weakens the flux at the trailing pole tip	
(D) none of the above 243. What is full form of THD in the context of inverter output waveform? (A) Total Harmonic Disorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Disorder 244. A converts a fixed voltage DC source into a AC source. (A) Inverter (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (C) Quantizing (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit (C) half adder circuit (D) full adder circuit (E) demultiplexer (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt		B) weakens the flux at the leading pole tip	
243. What is full form of THD in the context of inverter output waveform? (A) Total Harmonic Disorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Distortion (D) Theoretical Harmonic Distortion (D) Theoretical Harmonic Distorder 244. A converts a fixed voltage DC source into a AC source. (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt		(C) strengthens the flux at the leading pole tip	
(A) Total Harmonic Disorder (B) Theoretical Harmonic Distortion (D) Theoretical Harmonic Distortion (D) Theoretical Harmonic Disorder 244. A converts a fixed voltage DC source into a AC source. (A) Inverter (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (B) demultiplexer (C) half adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt		(D) none of the above	
Converts a fixed voltage DC source into a AC source. Allowerter (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (T) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt	243.	What is full form of THD in the context of inve	rter output waveform?
244. A converts a fixed voltage DC source into a AC source. (B) Rectifier (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt		(A) Total Harmonic Disorder	(B) Theoretical Harmonic Distortion
All Inverter (C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by All Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (B) demultiplexer (C) half adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt		C) Total Harmonic Distortion	(D) Theoretical Harmonic Disorder
(C) Chopper (D) Cycloconverter 245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (B) demultiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (T) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (E) 25 lumen/watt (D) 2.5 lumen/watt	244.	A converts a fixed voltage DC source i	nto a AC source.
245. Analog Signals can be converted into discrete time signals by (A) Sampling (B) Coding (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 251 umen/watt (D) 2.5 lumen/watt (E) 251 umen/watt (E) 251 umen/watt (E) 251 umen/matt		A)Inverter	(B) Rectifier
A) Sampling (C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt		(C) Chopper	(D) Cycloconverter
(C) Quantizing (D) None of the above 246. The number of pins in 8085 microprocessor are (A) 27 (B) 40 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (B) demultiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (E) 250 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt (D) 2.5 lumen/watt	245.	Analog Signals can be converted into discrete t	ime signals by
246. The number of pins in 8085 microprocessor are (A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (B) demultiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 25 lumen/watt		(A) Sampling	(B) Coding
(A) 27 (C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (T) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt Estimate of the carry is a carry and yield a carry is a carry and yield a carry is a laminous flux of support in the same of the flux of the flux of the flux of the same of the flux of		(C) Quantizing	(D) None of the above
(C) 15 (D) 36 247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit (D) full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged	246.	The number of pins in 8085 microprocessor are	
247. The combinational circuit that can add two binary numbers, accept a carry and yield a carry is a (A) multiplexer (C) half adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(A) 27	(B) 40
(A) multiplexer (C) half adder circuit D full adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled D be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt Solution (B) remains unchanged		(C) 15	(D) 36
(C) half adder circuit 248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged	247.	The combinational circuit that can add two bin	ary numbers, accept a carry and yield a carry is a
248. If the flux per pole of the d.c generator is halved but, its speed is doubled, its generated emf will (A) be halved (B) remain the same (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(A) multiplexer	(B) demultiplexer
(A) be halved (C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt (E) 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(C) half adder circuit	(D) full adder circuit
(C) be doubled (D) be quadrupled 249. In an 8085 microprocessor, after the execution of XRAA instruction (A) The carry flag is set (B) The accumulator contains FFH (The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged	248.	If the flux per pole of the d.c generator is halve	d but, its speed is doubled, its generated emf will
249. In an 8085 microprocessor, after the execution of XRA A instruction (A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(A) be halved	(B) remain the same
(A) The carry flag is set (B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(C) be doubled	(D) be quadrupled
(B) The accumulator contains FFH (C) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged	249.	In an 8085 microprocessor, after the execution	of XRAA instruction
(D) The zero flag is set (D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(A) The carry flag is set	
(D) The accumulator contents are shifted left by one bit 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(B) The accumulator contains FFH	
 250. A 60 W lamp, given a luminous flux of 1500 lumen will have an efficiency of (A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged 		C) The zero flag is set	
(A) 1500 lumen/watt (B) 250 lumen/watt (C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(D) The accumulator contents are shifted left b	y one bit
C) 25 lumen/watt (D) 2.5 lumen/watt 251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged	250.	A 60 W lamp, given a luminous flux of 1500 lur	nen will have an efficiency of
251. When the load on the transformer is increased, the eddy current (A) is increased (B) remains unchanged		(A) 1500 lumen/watt	(B) 250 lumen/watt
(A) is increased (B) remains unchanged		C) 25 lumen/watt	(D) 2.5 lumen/watt
	251.	When the load on the transformer is increased	the eddy current
(C) is decreased (D) becomes zero		(A) is increased	(B) remains unchanged
		(C) is decreased	(D) becomes zero

252.	Bundled conductors are mainly used in high voltage overhead transmission lines to		
	(A) reduce transmission line losses	(B) increase mechanical strength of the line	
	C) reduce corona	(D) reduce sag	
253.	It is desirable that voltage regulation of a trans	smission line should be	
	(A) high	(B) low	
	(C) 90%	(D) infinite	
254.	The 2's complement representation of (– 17) is		
	(A) 01110	(B) 01111	
	C)11110	(D) 10001	
255.	If a JK flip flop toggles more than once during	one clock cycle, it is called	
	(A) Bouncing	(B) Racing	
	(C) Pinging	(D) Spiking	
256.	Cycloconverter converts		
	(A) Fixed dc to variable ac	(B) Fixed dc to variable dc	
	(C) Fixed ac to variable dc	(D) Fixed ac to variable ac	
257.	What is mean by ALU?		
	(A) Arithmetic logic upgrade	(B) Arithmetic logic unsigned	
	(C) Arithmetic local unsigned	(D)Arithmetic logic unit	
258.	is the process of turning off a thyristor.		
	(A) Commutation	(B) Triggering	
	(C) Firing	(D) Latching	
259.	Regenerative braking mode can be achieved in which quadrant (V-I curve)?		
	(A) Third	(B) Second	
	(C) Fourth	(D) First	
260.	Type-A chopper is used for obtaining which type of mode?		
	A) Motoring mode	(B) Regenerative braking mode	
	(C) Reverse motoring mode	(D) Reverse regenerative braking mode	
261.	In a double cage induction motor, good starting	g torque is produced because at starting,	
	(A) Impedance of the outer winding is less than that of the inner winding, causing a large portion of the current to flow through the outer winding		
	(B) Impedance of the outer winding is more than that of the inner winding, causing a large portion of the current to flow through the outer winding		
	(C) Impedance of the inner winding is less that of the current to flow through the inner win	n that of the outer winding, causing a large portion nding	
	(D) Impedance of the inner winding is more that of the current to flow through the inner win	nn that of the outer winding, causing a large portion	

- 262. In an autotransformer, the primary and secondary are
 - (A) only magnetically coupled

- (B) only electrically coupled
- (C) magnetically as well as electrically
- (D) not coupled at all
- 263. The transfer function is defined as
 - (A) The ratio of Laplace transform of output to Laplace transform of input considering initial condition as zero.
 - (B) The ratio of Laplace transform of input of Laplace transform to output considering initial condition as zero.
 - (C) The ratio of input to output
 - (D) The ratio of error to input
- 264. Unit impulse response of a system in Laplace transform form gives
 - (A) Transfer function

(B) System gain

(C) Unit step function

(D) Unit ramp function

- 265. For a stable system
 - (A) Gain Margin & Phase Margin both are positive
 - (B) Gain Margin & Phase Margin both are negative
 - (C) Gain Margin positive & Phase Margin both are negative
 - (D) Gain Margin negative & Phase Margin both are positive
- 266. The corona effect is
 - (A) The air surrounding the conductor becomes conducting and as a result, the virtual diameter of the conductor is decreased
 - (B) The air surrounding the conductor is unaffected and there is no change in the virtual diameter of the conductor
 - (C) The air surrounding the conductor becomes conducting and as a result, the virtual diameter of the conductor is increased
 - (D) The air surrounding the conductor is unaffected but, there is a decrease in the virtual diameter of the conductor.
- 267. In a SCR, for dv/dt protection with RC circuit is known as
 - (A) Crowbar Circuit

(B) Turn on Circuit

(C) Snubber Circuit

- (D) Turn off Circuit
- 268. What is full form of GTO in context of thyristor classification?
 - (A) Gate turn on Thyristor

(B) Gate trigger on Thyristor

(C) Gate testing on Thyristor

- (D) Gate turn off Thyristor
- 269. A closed loop control system has the characteristic equation given by $s^3 + 4.5 s^2 + 3.5 s + 1.5 = 0$. Comment upon the stability using Routh Hurwitz criterion.
 - (A) System is stable

(B) System is unstable

(C) System is marginally stable

(D) System is critically stable

270.	. Which type of chopper is known as four quadrant chopper?	
	(A) Class A Chopper	(B) Class B Chopper
	(C) Class D Choppper	(D) Class E Chopper
271.	An ideal current source has zero	
	(A) internal conductance	(B) internal resistance
	(C) voltage on no load	(D) ripple
272.	(52)10 = () 2	
	(A) (110110) 2	(B) (110101) 2
	(C)(110100) 2	(D) (100100) 2
273.	At maximum power point of the solar cell	
	(A) current is maximum	
	(B) voltage is maximum	
	(C) both voltage and current are maximum	
	(D) the product of voltage and current is maxim	num
274.	Which of the following is known as Universal G	fate?
	(A) OR	(B) NOT
	(C) AND	DNOR
275.	What is the maximum number of inputs a NOT	gate can have?
	(A) 1	(B) 2
	(C) 3	(D) 4
276.	The device commonly used for triggering a TRI	AC is a
	(A) Diode	B) Diac
	(C) Transistor	(D) Thyristor
277.	If the output of a rectifier is pure DC, then the	ripple factor will be
	(A) 0	(B) 1
	(C) 1.21	(D) 0.48
278.	The minimum current below which a thyristor	stops conduction is known as the
	(A) Saturation Current	(B) Gate Current
	(C) Electron Current	D) Holding Current
279.	In a critically damped system,	
	(A) oscillations are prominent	(B) no oscillations are observed
	(C) oscillations just disappear	(D) oscillations are sustained
280.	Equalizer circuits are provided across each SCI	R in series operation to provide uniform
	(A) current distribution	B) voltage distribution
	(C) firing of SCRs	(D) all of the above

291.	CPU stands for	
	(A) Common Purpose Unit	(B) Central Processing Unit
	(C) Central Point Unit	(D) Common Processing Unit
292.	The value of the intrinsic stand off ratio for the	UJT lies between
	(A) Between 0 and 0.3	(B) Between 1 and 2
	(C) Zero	(D) Between 0.51 and 0.82
293.	The air gap in an alternator, as compared to an	induction motor is
	(A) much shorter	(B) much longer
	(C) about the same	(D) zero
294.	When the varying frequncy of an ac motor is circuit on and off several time during each half	produced by rapidly switching the output of the cycle, it is referred to as
	A) Pulse width modulation	(B) Pulse width control
	(C) Pulse Amplitude modulation	(D) Pulse amplitude control
295.	While increasing the value of the gain factor K	, the system becomes
	A) less stable	(B) more stable
	(C) unstable	(D) absolutely stable
296.	In which year Gujarat state government has an	nnounced wind solar hybrid policy?
	A)2018	(B) 2019
	(C) 2020	(D) 2021
297.	A 3-phase induction machine draws active por machine is operated as a generator, P and Q with	wer P and reactive power Q from the grid. If this
	(A) positive and negative	(B) positive and positive
	(C) negative and negative	(D) negative and positive
298.	In HVDC, VSC schemes filters are used	
	A) Only on the AC side	(B) Only on the DC side
	(C) Both AC and DC side	(D) No filter is needed
299.	The maximum value of the harmonic current of	lepends on
	(A) Firing Angle	(B) Overlap Angle
	(C) DC current	(D) Both firing and overlap angle
300.	The ground currents in HVDC system flow thr	ough
	(A) Small Area	
	(B) Small Area along the line	
	C) Very large area and do not confine to the ro	oute of the line
	(D) Very large area along the route of the line	